

Electrical Engineering

HSLU, Semester 2

Matteo Frongillo

Last update:

March 24, 2025

Contents

| | | |
|----------|----------------------------------------------------|----------|
| I | ... | 3 |
| 1 | ... | 3 |
| 1.1 | Current strength or current “I” | 3 |
| 1.2 | Current density “J” | 3 |
| 1.3 | Temperature dependence of the resistance | 3 |
| 1.4 | Object properties | 4 |
| 1.5 | Reciprocal quantities | 4 |
| 1.5.1 | Specific resistance | 4 |
| 1.5.2 | Conductance | 4 |
| 1.5.3 | Specific conductivity | 4 |
| 2 | Gravitational fields | 5 |
| 2.1 | Between bodies | 5 |
| 2.2 | Between particles | 5 |
| 2.2.1 | Coulomb’s law | 5 |
| 2.3 | Electric field and force on a charge Q | 5 |
| 2.3.1 | Homogeneous electric fields | 5 |
| 2.3.2 | Force on a point charge | 5 |
| 3 | Capacitance and Capacitor | 6 |
| 3.1 | Capacitor | 6 |
| 3.2 | Capacitance | 6 |
| 3.2.1 | Capacitance of a plate capacitor | 6 |
| 3.2.2 | Energy in a capacitor | 6 |
| 3.3 | Capacitors in parallel connection | 7 |
| 3.4 | Capacitors in series connection | 7 |
| 4 | Transient Analysis in RC Circuits | 7 |
| 4.1 | Charging of a Capacitor | 7 |
| 4.2 | Discharging of a Capacitor | 7 |
| 4.3 | Transitional phase | 8 |
| 5 | Additional Topics | 8 |
| 5.1 | Energy Stored in a Capacitor | 8 |
| 5.2 | Charge–Voltage Relationship | 8 |
| 6 | Electromagnetic fields | 9 |
| 6.1 | Hans Christian Ørsted Observation | 9 |
| 6.2 | Definitions and formuals | 9 |
| 6.2.1 | Magnetomotive force | 9 |
| 6.2.2 | Ampère’s circuital law | 9 |
| 6.2.3 | Magnetic field in a coil | 9 |
| 6.2.4 | Magnetic flux density | 10 |


| | | |
|----------|-------------------------------------------------------------------------|-----------|
| 6.2.5 | Magnetic field strength in coil with iron core | 10 |
| 6.2.6 | Magnetic relative permeability μ | 10 |
| 6.2.7 | Coils with and without iron core | 11 |
| 6.2.8 | Law of induction and inductance | 11 |
| 6.2.9 | Inductance and induction | 12 |
| 6.2.10 | Inductivity of a very long coil | 12 |
| 6.2.11 | Energy stored in an inductor | 12 |
| 6.2.12 | Current-voltage relationship of an inductor | 13 |
| 6.2.13 | Transient analysis | 13 |
| 6.3 | Examples | 14 |
| 6.3.1 | Charging an inductor in a RL-network | 14 |
| 6.3.2 | Discharging an inductor in a RL-network | 15 |
| 7 | Alternating current (AC) | 16 |
| 7.1 | Generation of alternating current / voltage | 16 |
| 7.2 | Comparison of AC and DC | 16 |
| 7.2.1 | Advantages of AC | 16 |
| 7.2.2 | Disadvantages of AC | 16 |
| 7.3 | Phasors | 16 |
| 7.4 | Oscillation as a function of the angle | 17 |
| 7.5 | Zero phase angle φ | 17 |
| 7.5.1 | Phase shift $\Delta\varphi$ between two signals | 17 |
| 7.6 | Power in a sinusoidal signal and effective value | 17 |
| 7.6.1 | Instantaneous power | 17 |
| 7.6.2 | Effective value | 18 |
| 7.7 | Relationship between current and voltage on a capacitor | 18 |
| 7.8 | Capacitive reactance X_c | 18 |
| 7.9 | Relationship between current and voltage on an ideal inductor | 19 |
| 7.10 | Inductive reactance X_L | 19 |

Part I

...


1 ...

1.1 Current strength or current “I”

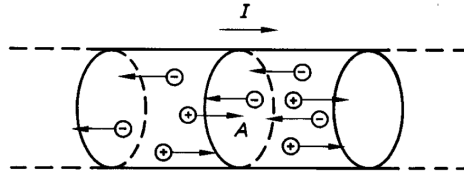

$$I [A] = \frac{\text{el. charge}}{t}$$


1.2 Current density “J”

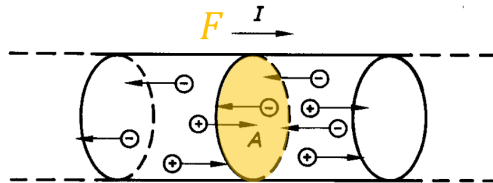

The current density indicates how large the current per cross-sectional area (F) is:

$$J \left[\frac{A}{mm^2} \right] = \frac{I}{F}$$

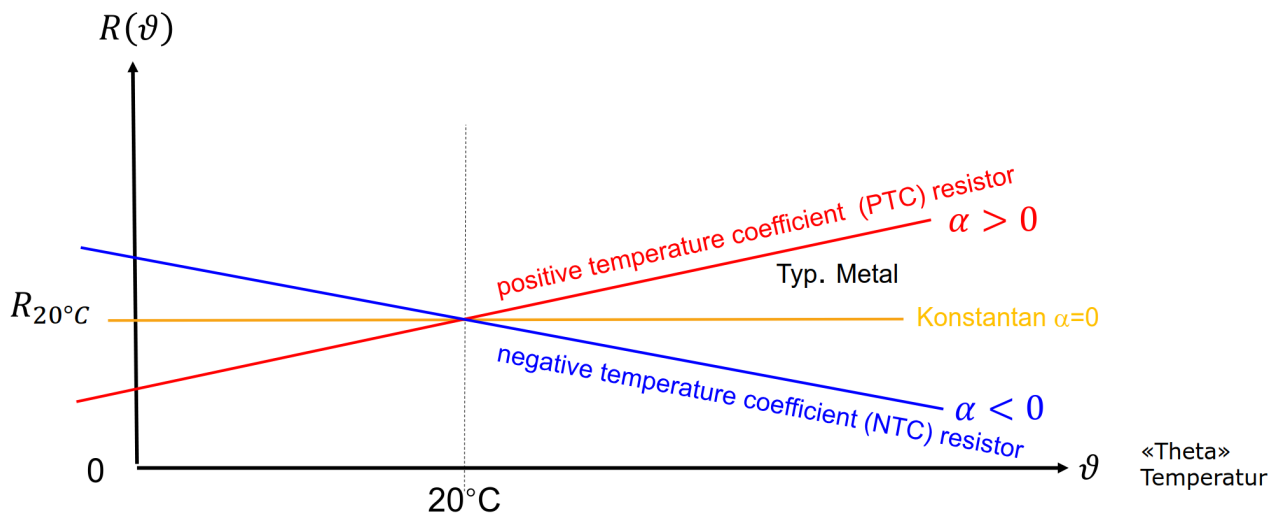1.3 Temperature dependence of the resistance



Depending on the material, the resistance can increase, remain the same or decrease with temperature. In ET+L we calculate using the linear approach.

$$R(\vartheta) = R_{20}(1 + \alpha(\vartheta - 20^\circ\text{C})) = R_{20}(1 + \alpha\Delta T)$$

1.4 Object properties

The resistance indicates the voltage required for a current. In addition to the material, the cross-sectional area and also the length are decisive factors.

$$R = \frac{U}{I}$$

1.5 Reciprocal quantities

1.5.1 Specific resistance

To describe material properties, the resistance per length and cross-sectional area is specified (precondition: homogeneous conductor, direct current):

$$\rho \left[\frac{\Omega \cdot \text{mm}^2}{\text{m}} \right] = R \cdot \frac{A}{l}$$

1.5.2 Conductance

1.5.3 Specific conductivity

2 Gravitational fields

2.1 Between bodies

$$F_1 = F_2 = G \frac{m_1 m_2}{d^2}$$

2.2 Between particles

2.2.1 Coulomb's law

It calculates the amount of force between two electrically charged particles at rest:

$$F = \frac{1}{4\pi\epsilon_0} \cdot \frac{q_1 q_2}{r^2}$$

where:

- F : Force [N];
- q : Charge [As];
- ϵ_0 : absolute permittivity = $8.8542 \cdot 10^{-12}$ [As/Vm].

2.3 Electric field and force on a charge Q

2.3.1 Homogeneous electric fields

$$E = \frac{U}{d}$$

where:

- E : electric field strength [V/m];
- U : voltage [V];
- d : distance of the electrodes [m].

2.3.2 Force on a point charge

$$F = Q \cdot E$$

where:

- E : electric field strength [V/m];
- Q : charge [As];
- F : force [N].

3 Capacitance and Capacitor

3.1 Capacitor

A capacitor is a device in which the capacitance is used.

3.2 Capacitance

Capacitance C is the **capability** to store electric charge. It is measured by the charge divided by the applied voltage:

$$C = \frac{Q}{U}$$

where:

- Q : charge [As];
- U : voltage [V];
- C : capacitance [As/V = F (Farad)].

3.2.1 Capacitance of a plate capacitor

$$C = \varepsilon \cdot \frac{A}{d}$$

where:

- A : plate area (one side) [m²];
- d : distance between plates [m];
- C : capacitance [F].

Permittivity

$$\varepsilon = \varepsilon_r \cdot \varepsilon_0$$

- ε_r : relative permittivity of the dielectric, relative to the air;
- ε_0 : absolute permittivity [As/Vm].

3.2.2 Energy in a capacitor

If a capacitor is discharged with a constant current, the voltage decreases linearly:

$$\int_0^{t_{\text{empty}}} U(t) \cdot I \, dt = I \cdot U_0 = \frac{I \cdot U_0 \cdot t_{\text{empty}}}{2}$$

Or, simplified:

$$W = \frac{1}{2} C \cdot U_0^2$$

where:

- W : energy [J or Ws];
- U_0 : initial voltage [V];
- C : capacitance [F].

3.3 Capacitors in parallel connection

Capacitances connected in parallel add up:

$$C_{\text{tot}} = \frac{\sum_n Q_n}{U} = \sum_n C_n$$

or

$$C = \frac{\varepsilon \cdot (\sum_n A_n)}{d} = \sum_n C_n$$

3.4 Capacitors in series connection

In a series connection, the reciprocal of the total capacitance is the sum of the reciprocals of the individual capacitances:

$$\frac{1}{C_{\text{tot}}} = \sum_n \frac{1}{C_n}$$

where:

- C_{tot} : total capacitance [F];
- C_n : capacitance of the n -th capacitor [F].

4 Transient Analysis in RC Circuits

4.1 Charging of a Capacitor

When a capacitor is charged through a resistor, the voltage across it increases exponentially:

$$U_C(t) = U_0 \cdot \left(1 - e^{-t/(R \cdot C)}\right)$$

with the time constant defined as:

$$\tau = R \cdot C$$

where:

- $U_C(t)$: voltage across the capacitor at time t [V];
- U_0 : applied voltage [V];
- R : resistance [Ω];
- C : capacitance [F];
- τ : time constant [s].

4.2 Discharging of a Capacitor

When a charged capacitor discharges through a resistor, the voltage decays exponentially:

$$U_C(t) = U_0 \cdot e^{-t/(R \cdot C)}$$

and the discharging current is:

$$I(t) = \frac{U_0}{R} \cdot e^{-t/(R \cdot C)}$$

4.3 Transitional phase

$$f(t) = A + \Delta \cdot (1 - e^{t/\tau}) = A + (B - A) \cdot (1 - e^{1/\tau})$$

5 Additional Topics

5.1 Energy Stored in a Capacitor

The energy stored in a capacitor is given by:

$$W = \frac{1}{2} C \cdot U_0^2$$

where:

- W : energy [J];
- C : capacitance [F];
- U_0 : voltage [V].

5.2 Charge–Voltage Relationship

For an ideal capacitor, the relationship between charge and voltage is:

$$Q = C \cdot U$$


Moreover, the current is the time derivative of the charge:

$$I = \frac{dQ}{dt} = C \cdot \frac{dU}{dt}$$

Note that the voltage across an ideal capacitor cannot change instantaneously.

6 Electromagnetic fields

6.1 Hans Christian Ørsted Observation

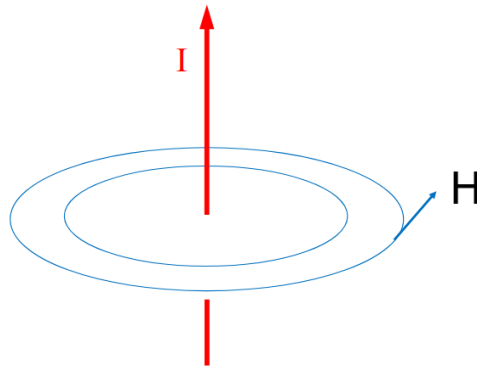

1. The magnetic field lines encircle the current-carrying conductor;
2. The magnetic field lines lie in a plane perpendicular to the current-carrying wire;
3. If the direction of the current is reversed, the direction of the magnetic field lines is also reversed;
4. The strength of the field is directly proportional to the magnitude of the current;
5. The strength of the field at any point is inversely proportional to the distance of the point from the wire.

6.2 Definitions and formuals


6.2.1 Magnetomotive force

$$\theta = N \cdot I$$

6.2.2 Ampère's circuital law

$$\theta = \oint \vec{H}(s) \cdot d\vec{s}$$

6.2.3 Magnetic field in a coil

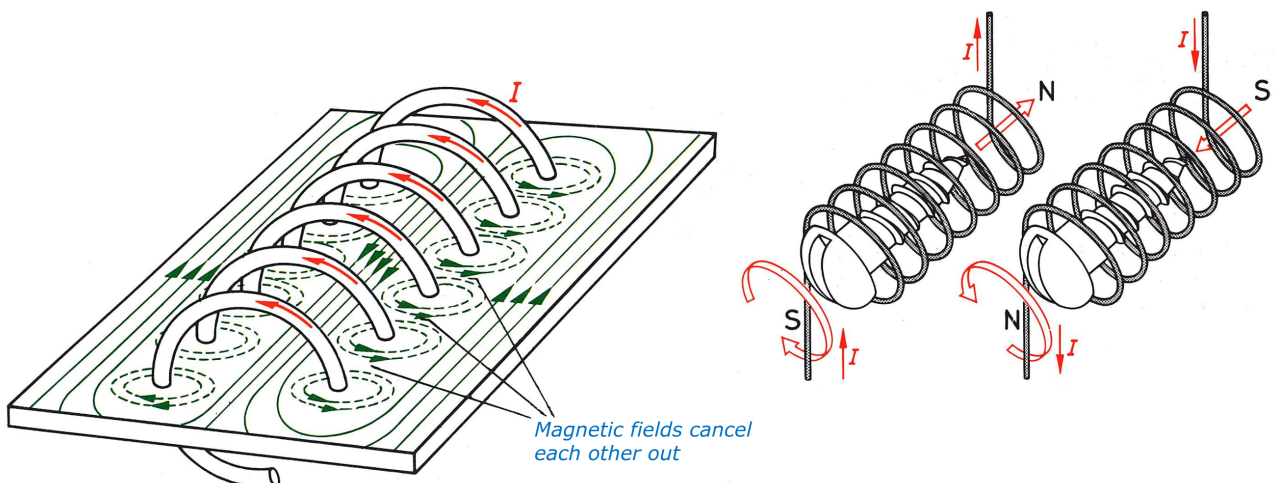

6.2.4 Magnetic flux density


$$B = \frac{\Phi}{A} = \mu \cdot H = \mu_0 \mu_r \cdot H$$

where:

- B : magnetic flux density [T = Vs/m²];
- Φ : magnetic flux [Wb];
- A : area [m²];
- μ : magnetic permeability [H/m = Vs/Am];
- H : magnetic field strength [A/m];
- μ_0 : magnetic constant [$4\pi \cdot 10^{-7}$ Vs/Am];
- μ_r : relative permeability.

Note: Φ is the sum of all B-field lines through the cross section A

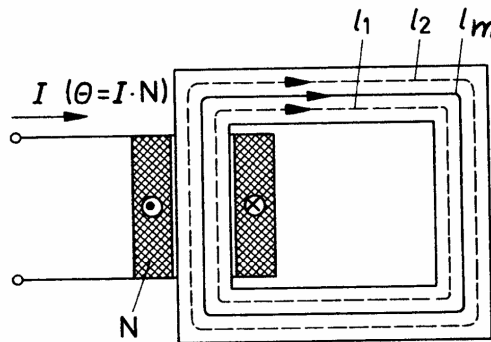6.2.5 Magnetic field strength in coil with iron core



$$H = \frac{N \cdot I}{l_m} = \frac{\Theta}{l_m}$$

where:

- H : magnetic field strength [A/m];
- N : number of turns;
- I : current [A];
- l_m : median field line length [m];
- Θ : magnetomotive force [A].




6.2.6 Magnetic relative permeability μ

Permeability is a measure for the ability to conduct magnetic field lines:

| Material | μ_r |
|------------------|---------------|
| Air | 1 |
| Pure iron | up to 250'000 |
| Electrical steel | 500 ... 7000 |
| Steel | 40 ... 7000 |
| Water | 0.99991 |

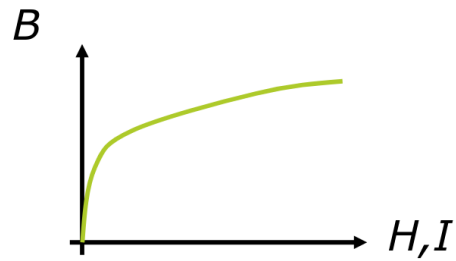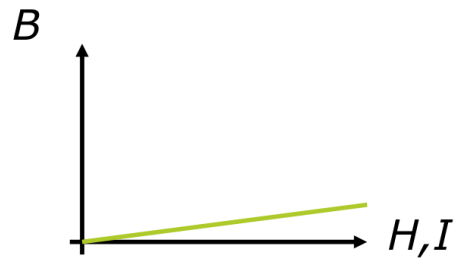
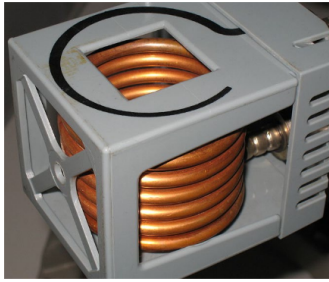
6.2.7 Coils with and without iron core

The magnetization curve of a coil without a core is linear, but there is significantly less flux density B than with an iron core.



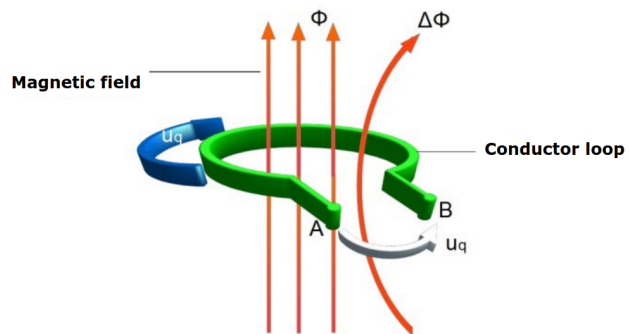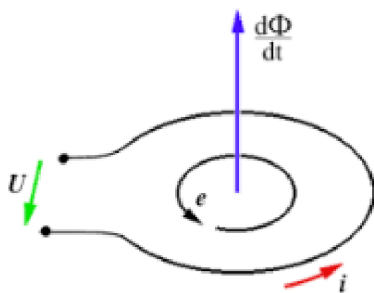6.2.8 Law of induction and inductance

Changing magnetic flux generates a voltage



Phenomenon: a changing magnetic flux Φ induces a voltage in a conductor loop around it:

$$U = -N \cdot \frac{d\Phi}{dt}$$

6.2.9 Inductance and induction

Inductance L is the capability to generate a magnetic field. It is measured by the voltage divided by the rate of change of current over time. It is a measure of the magnetic “capacity” of an arrangement of conductors (e.g. coil) and can be compared to the capacity C of a capacitor. It indicates how much magnetic flux per ampere is generated.

$$L = \frac{N \cdot \Phi}{I} = \frac{U}{\frac{\Delta I}{\Delta t}}$$

where:

- L : inductance [$\text{H} = \text{Vs/A}$];
- N : number of turns;
- Φ : magnetic flux [Wb];
- I : current [A];
- U : voltage [V].

6.2.10 Inductivity of a very long coil

The inductance of a very long coil can be calculated approximately with:

$$L = \frac{\mu \cdot N^2 \cdot A}{l}$$

where:

- L : inductance [$\text{H} = \text{Vs/A}$];
- μ : magnetic permeability [Vs/Am];
- N : number of turns;
- A : cross-section of the coil [m^2];
- l : length [m].

6.2.11 Energy stored in an inductor

Since a variable magnetic field induces a voltage in which a current can also flow, the magnetic field must contain energy:

$$W = \frac{1}{2} L \cdot I^2$$

where:

- W : work, energy [$\text{J} = \text{Ws}$];
- L : inductance [$\text{H} = \text{Vs/A}$];
- I : current [A].

6.2.12 Current-voltage relationship of an inductor


The current-voltage relationship of an inductor is:

$$U = L \cdot \frac{dI}{dt}$$

Special case:

$$0 = L \cdot \frac{dI}{dt} \rightarrow u_c = 0$$

6.2.13 Transient analysis

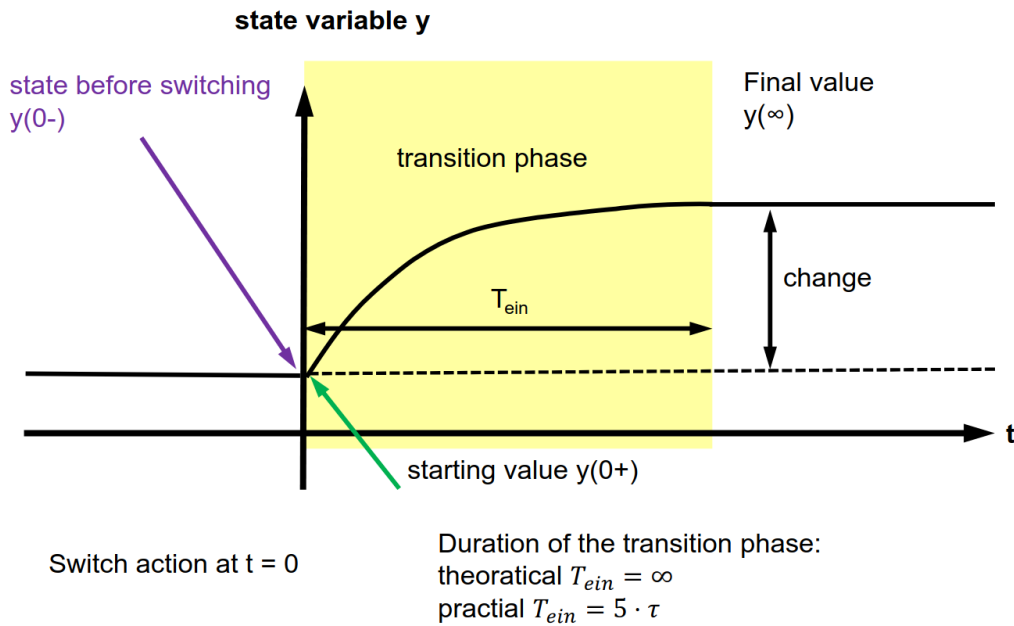

1. The state variable $y(t)$ is the variable that cannot change instantaneously. For the inductor, this is $i_L(t)$. The state just before the switch action:

$$y(0^-) = i_L(0^-).$$

2. The starting value is the state immediately before the switch action:

$$y(0^+) = i_L(0) = i_L(0^-).$$

That is, the state variable i_L keeps the value from $t = 0^-$.

3. The final value is the value long after the switch action:

$$y(\infty) = i_L(\infty),$$

which is practically reached after 5τ .

4. The transient is described by the function of time:

$$y(t) = \text{final value} + (\text{starting value} - \text{final value}) \exp\left(-\frac{t}{\tau}\right).$$

Hence,

$$i_L(t) = i_L(\infty) + (i_L(0+) - i_L(\infty)) \exp\left(-\frac{t}{\tau}\right).$$

Time constant τ for an inductor


$$\tau = \frac{L}{R}$$

where:

- τ : time constant [s];
- L : inductance [H];
- R : resistance [Ω].

6.3 Examples

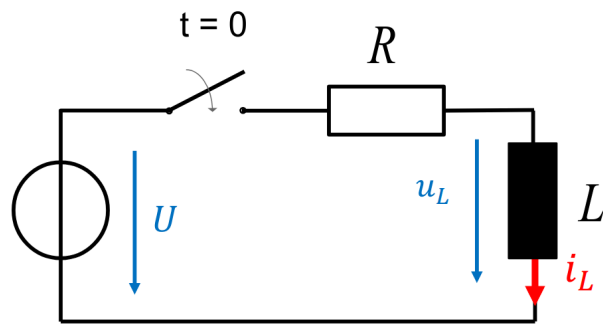6.3.1 Charging an inductor in a RL-network




For $t < 0$ stationary state, L discharged


Calculations

$$i_L = \frac{U}{R} \cdot \left(1 - \exp\left(-\frac{t}{\tau}\right)\right)$$
$$u_L = U \cdot \exp\left(-\frac{t}{\tau}\right)$$

Graphical representation

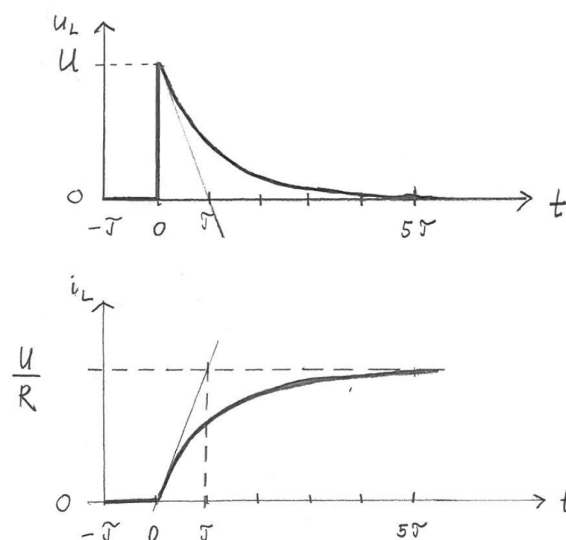

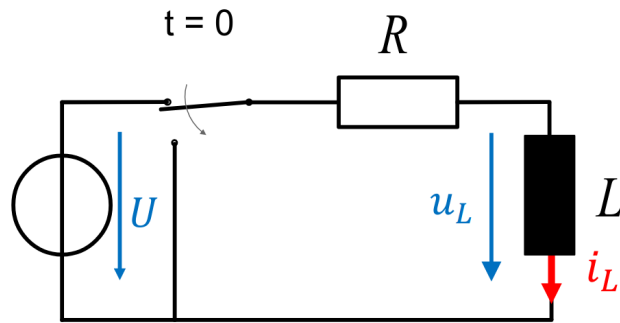6.3.2 Discharging an inductor in a RL-network





Before $t = 0$ stationary state:
Current in inductor is I_0

Calculations

$$i_L = I_0 \cdot \exp\left(-\frac{t}{\tau}\right)$$

$$u_L = -I_0 \cdot R \cdot \exp\left(-\frac{t}{\tau}\right)$$

Graphical representation

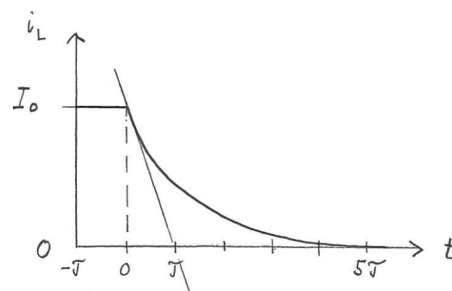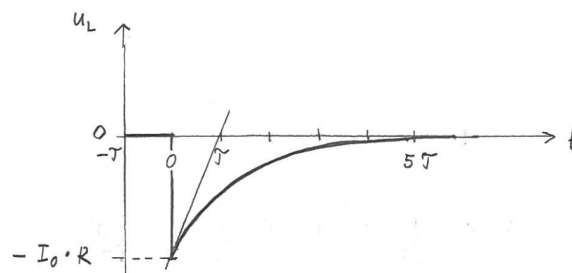

7 Alternating current (AC)



7.1 Generation of alternating current / voltage

$$U = -N \cdot \frac{\Delta\Phi}{\Delta t}$$

where:

- U : voltage [V];
- N : number of turns;
- Φ : magnetic flux [Wb].

7.2 Comparison of AC and DC

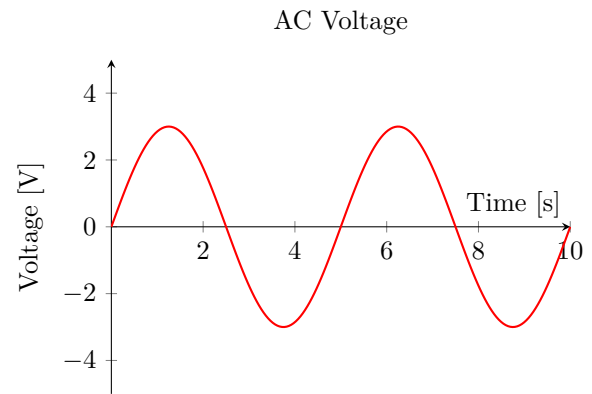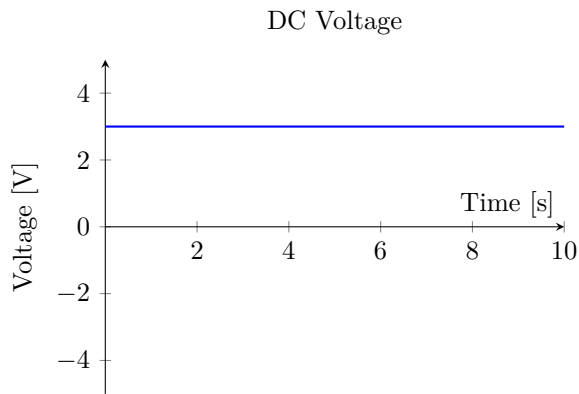


7.2.1 Advantages of AC

- Simple voltage transformation;
- Efficient transmission;
- Easier generation;
- Compatibility with electric motors.

7.2.2 Disadvantages of AC

- Complexity in storage;
- Higher risk of shock;
- Complex circuits;
- Higher rectification costs.

7.3 Phasors

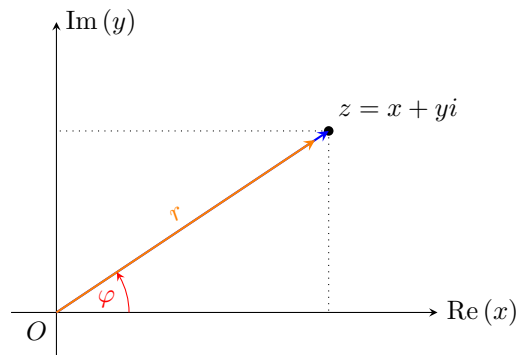

$$z = x + yi = r \angle \varphi$$

7.4 Oscillation as a function of the angle

Sinusoidal voltage has an instantaneous value $u(t)$ or u for every time t .

After a period of time T , the curve repeats itself.

$$u(t) = \hat{U} \sin(\omega \cdot t)$$

7.5 Zero phase angle φ


$$u(t) = \hat{U} \sin(\omega \cdot t + \varphi_u)$$

7.5.1 Phase shift $\Delta\varphi$ between two signals

$$\begin{aligned} u(t) &= \hat{U} \sin(\omega \cdot t + \varphi_u) \\ i(t) &= \hat{I} \sin(\omega \cdot t + \varphi_i) \end{aligned}$$

The phase shift between two signals is the difference between the their zero phase signals:
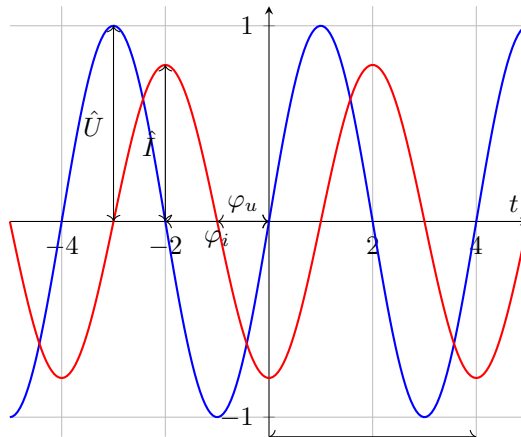
$$\Delta\varphi = \varphi_u - \varphi_i$$



7.6 Power in a sinusoidal signal and effective value

7.6.1 Instantaneous power

The instantaneous power $p(t)$ is the actual power at a specific time t and is the product of the voltage $u(t)$ and the current $i(t)$ at that moment:

$$p(t) = u(t) \cdot i(t) = \frac{u(t)^2}{R} = i(t)^2 \cdot R$$

The active power P corresponds to the mean value of the instantaneous power $p(t)$ averaged over a period T :

$$P = \frac{1}{T} \int_0^T p(t) dt$$

7.6.2 Effective value


The effective value U_{eff} of a sinusoidal signal is the voltage that would generate the same power in a resistor as the sinusoidal signal:

$$U_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T u(t)^2 dt} = \frac{\hat{U}}{\sqrt{2}}$$

The same can be applied to the effective value I_{eff} :



$$I_{\text{eff}} = \frac{\hat{I}}{\sqrt{2}}$$

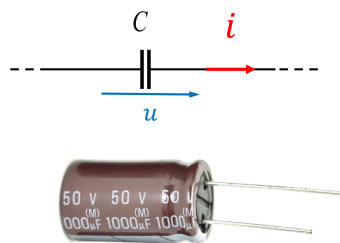7.7 Relationship between current and voltage on a capacitor



$$i = C \cdot \frac{\Delta u}{\Delta t}$$

7.8 Capacitive reactance X_c

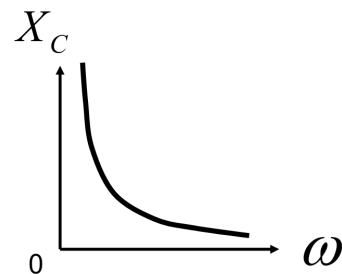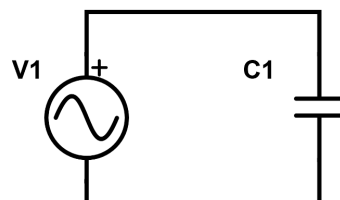


$$X_c = \frac{1}{\omega \cdot C}$$

where:



- X_c : capacitive reactance [Ohm];
- ω : angular frequency [rad/s];
- C : capacitance [F = As/V].

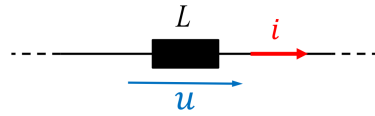7.9 Relationship between current and voltage on an ideal inductor



$$u = L \cdot \frac{\Delta i}{\Delta t}$$

7.10 Inductive reactance X_L

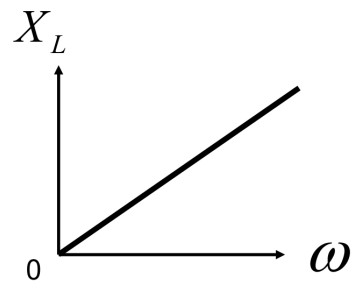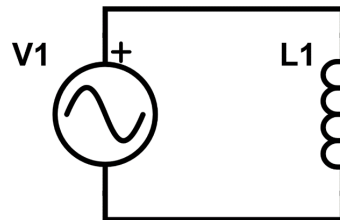

$$X_L = \omega \cdot L$$

where:

- X_L : inductive reactance [Ohm];
- L : inductance [H];
- ω : angular frequency [rad/s];